

KGC (03) – 4109 ✓

(REVISION – 2003)

KERALA GOVERNMENT CERTIFICATE EXAMINATION IN  
ELECTRICAL ENGINEERING — JUNE, 2016

BASIC ELECTRICAL AND ELECTRONICS

[Time : 3 hours

(Maximum marks : 100)

PART — A

(Maximum marks : 20)

Marks

I Answer the following questions in one or two sentences.

1. Define resistance.
2. State Kirchhoff's current law.
3. Define reluctance.
4. What is R.M.S. value ?
5. What is rechargeable cell ?
6. Write the colour code of a 1K resistor.
7. What is a transformer ?
8. Write the full form of ACSR conductor.
9. Define slip in a 3 $\phi$  Induction motor.
10. State the purpose of starter in a motor.

(10  $\times$  2 = 20)

PART — B

(Maximum marks : 80)

(Answer any *five* full questions from the following)

- 11 (a) State and explain Kirchhoff's law. 8
- (b) Find the resistance of a 100w, 250 volt incandicent lamp. 8

OR

- III (a) Obtain the expression for resistors connected in parallel. 8
- (b) Explain the construction and working of a lead acid battery. 8

- (IV) (a) Define :
- |                                |                    |   |
|--------------------------------|--------------------|---|
| (i) Flux in a magnetic circuit | (iii) Flux density |   |
| (ii) m.m.f.                    | (iv) Ampere turns. | 8 |
- (b) Explain : (i) Self induction (ii) Mutual induction. 8
- OR
- V (a) State the relation between voltage and current (Line and phase) in a 3-phase Star and Delta connected system. 8
- (b) Draw the vector diagram and current in an R-L series circuit. 8
- (VI) (a) Compare Copper and Aluminium. 8
- (b) Explain the properties and uses of carbon. 8
- OR
- VII (a) Draw the B.H. curve of a soft magnetic material. 8
- (b) State Faraday's laws of electromagnetic induction. 8
- VIII (a) Explain the working of a Transformer on load. 8
- (b) State the working of a 3-phase induction motor. 8
- OR
- (IX) (a) Explain the insulation test of Transformer oil. 8
- (b) State the working of a DC motor. 8
- X (a) Explain the working of a half wave rectifier. 8
- (b) Draw the circuit diagram of a Zener voltage regulator. 8
- OR
- (XI) (a) Draw the energy band diagram of a conductor and explain. 8
- (b) Explain the operation of Bridge rectifier. 8

[മലയാള പരിഭാഷ]

പാർട്ട്—എ

(മാർക്ക് : 20)

I താഴെ കൊടുത്തിരിക്കുന്ന ചോദ്യങ്ങൾക്ക് ഒന്നോ രണ്ടോ വാക്യത്തിൽ ഉത്തരം എഴുതുക :

1. നിർവ്വചിക്കുക “പ്രതിരോധം”.
2. കിർച്ചോസിന്റെ കറന്റ് നിയമം എഴുതുക.
3. നിർവ്വചിക്കുക “റിലക്റ്റൻസ്”.
4. എന്താണ് ആർ. എം. എസ്. മൂല്യം ?
5. എന്താണ് റീചാർജ്ജബിൾ സെൽ ?
6. ഒരു കിലോ ഓം പ്രതിരോധത്തിന്റെ കളർകോഡ് എഴുതുക.
7. എന്താണ് ട്രാൻസ്ഫോർമർ ?

- 8. ACSR-ന്റെ പൂർണ്ണരൂപം എഴുതുക.
- 9. എന്താണ് മൂന്ന് ഫേസ് ഇൻഡക്ഷൻ മോട്ടോറിന്റെ സ്ലിപ്പ് എന്നു പറയുന്നത് ?
- 10. ഒരു മോട്ടോറിൽ സ്റ്റാർട്ടറിന്റെ ആവശ്യകത. (10×2 = 20)

പാർട്ട് — ബി  
(മാർക്ക് : 80)

(ഏതെങ്കിലും അഞ്ച് പൂർണ്ണ ചോദ്യങ്ങൾക്ക് ഉത്തരം എഴുതുക.)

- II (a) കിർച്ചോഫ്സ് നിയമം എഴുതുകയും വിവരിക്കുകയും ചെയ്യുക. 8
- (b) ഒരു 100w, 250v ഇൻകാൻഡിസന്റ് ലാമ്പിന്റെ പ്രതിരോധം കണ്ടുപിടിക്കുക. 8

അല്ലെങ്കിൽ

- III (a) പ്രതിരോധങ്ങൾ സമാന്തരമായി ഘടിപ്പിച്ചാൽ അതിന്റെ പരിണിത പ്രതിരോധത്തിന്റെ സൂത്രവാക്യം കണ്ടുപിടിക്കുക. 8
- (b) ഒരു ലെഡ് ആസിഡ് ബാറ്ററിയുടെ നിർമ്മാണവും പ്രവർത്തനവും വിവരിക്കുക. 8
- IV (a) നിർവ്വചിക്കുക. 8

  - (i) ഫ്ലൂക്സ് (ഒരു കാന്തികക്ഷേത്രത്തിലെ) (iii) ഫ്ലൂക്സ് ഡെൻസിറ്റി
  - (ii) എം. എം. എഫ്. (iv) ആമ്പിയർ ചുറ്റുകൾ

- (b) വിവരിക്കുക 8

  - (i) സെൽഫ് ഇൻഡക്ഷൻ (ii) മ്യൂച്ചൽ ഇൻഡക്ഷൻ

അല്ലെങ്കിൽ

- V (a) ഒരു മൂന്ന് ഫേസ് സ്റ്റാർ ബന്ധനത്തിലെയും, ഡെൽറ്റാ ബന്ധനത്തിലെയും കറന്റും വോൾട്ടതയും (ലെയ്നും ഫേസും) തമ്മിലുള്ള ബന്ധം എഴുതുക. 8
- (b) ഒരു R - L പരിപഥത്തിലെ കറന്റും വോൾട്ടതയും കാണിക്കുന്ന ചിത്രം വരയ്ക്കുക. 8
- VI (a) ചെമ്പിനെയും അലൂമിനിയത്തെയും താരതമ്യം ചെയ്യുക. 8
- (b) കാർബണിന്റെ ഗുണങ്ങൾ എഴുതുക. 8

അല്ലെങ്കിൽ

- VII (a) ഒരു സോഫ്റ്റ് കാന്തിക പദാർത്ഥത്തിന്റെ B.H കർവ് വരയ്ക്കുക. 8
- (b) ഫാരഡെയുടെ വൈദ്യുത കാന്തിക പ്രേരണ നിയമങ്ങൾ എഴുതുക. 8
- VIII (a) ഒരു ട്രാൻസ്ഫോർമറിന്റെ ലോഡിലെ പ്രവർത്തനം എഴുതുക. 8
- (b) ഒരു 3φ ഇൻഡക്ഷൻ മോട്ടോറിന്റെ പ്രവർത്തനം എഴുതുക. 8

അല്ലെങ്കിൽ

- IX (a) ട്രാൻസ്ഫോർമറിന്റെ ഓയിലിന്റെ ഇൻസുലേഷൻ ടെസ്റ്റ് ചെയ്യുന്ന രീതി വിവരിക്കുക. 8
- (b) ഒരു DC മോട്ടോറിന്റെ പ്രവർത്തനം എഴുതുക. 8
- X (a) ഒരു ഹാഫ് വേവ് റെക്ട്രിഫയറിന്റെ പ്രവർത്തനം വിവരിക്കുക. 8
- (b) സെനർ വോൾട്ടേജ് റെഗുലേറ്ററിന്റെ ചിത്രം വരയ്ക്കുക. 8

അല്ലെങ്കിൽ

- XI (a) ഒരു ചാലകത്തിന്റെ എനർജി ബാൻഡ് ചിത്രം വരച്ച് വിവരിക്കുക. 8
- (b) ഒരു Bridge rectifier ചിത്രം വരച്ച് പ്രവർത്തനം എഴുതുക. 8